
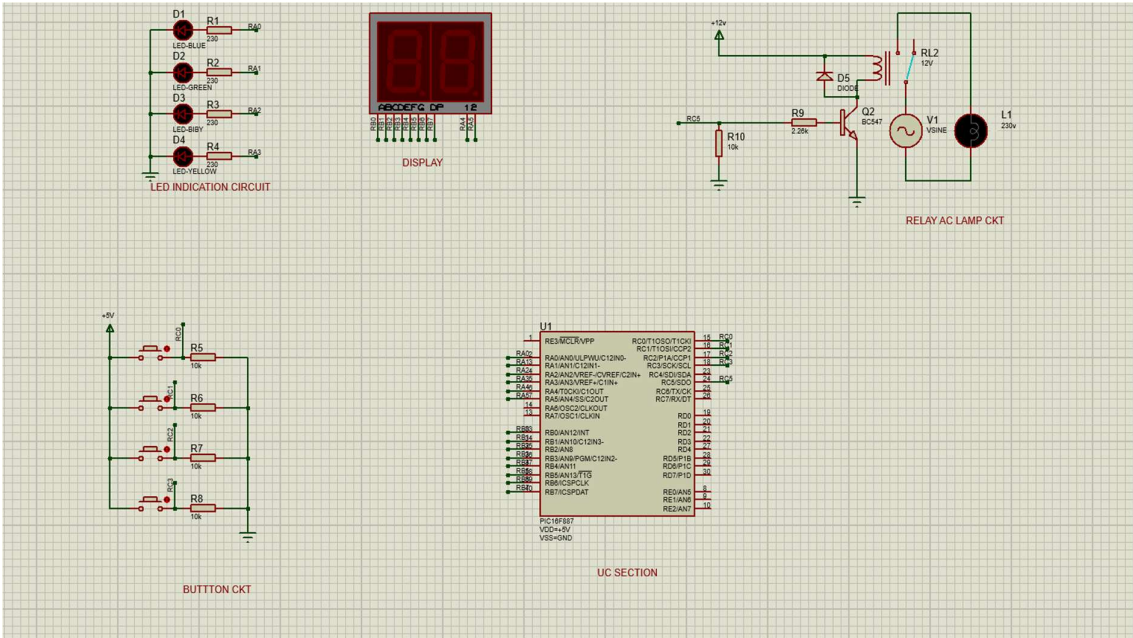



Circuit Diagram:

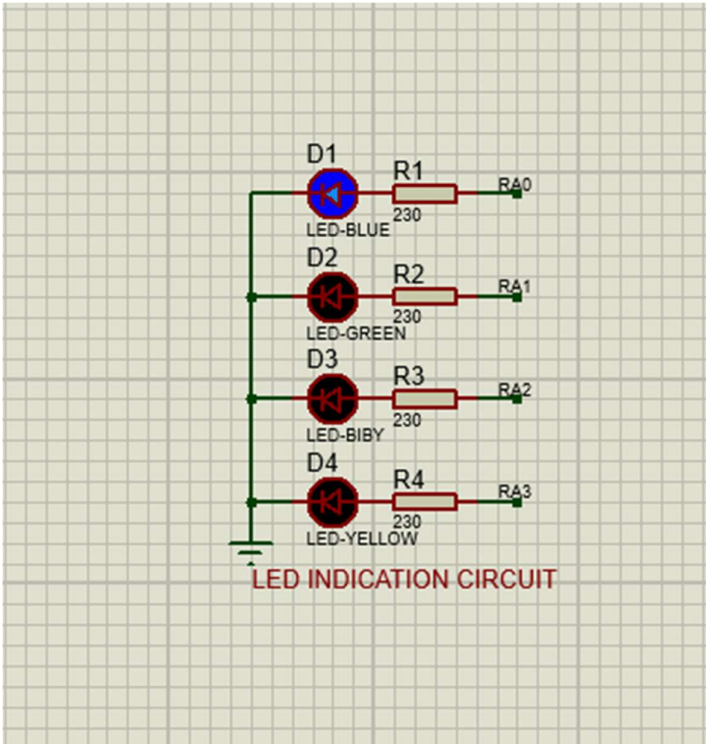


OUTPUTS:



LED 1 ON AT 1200MS

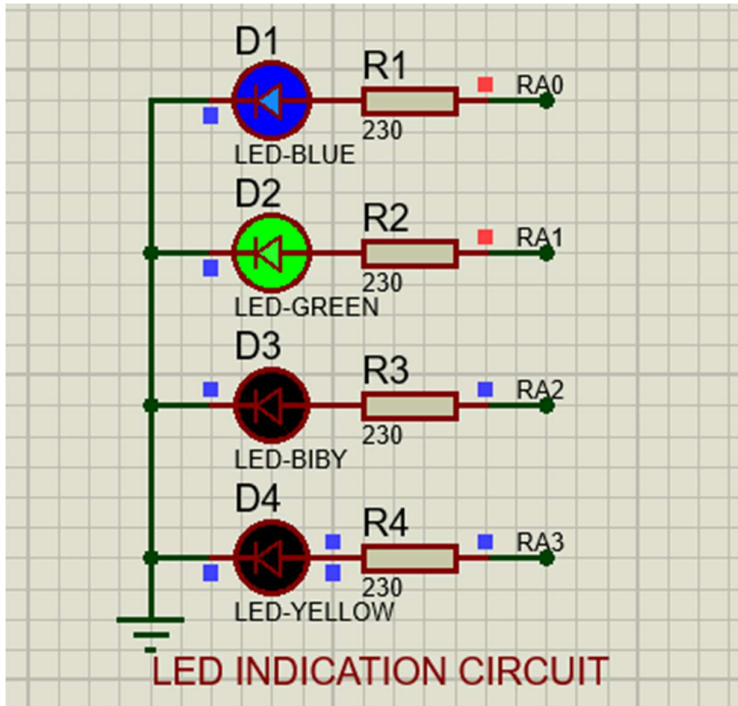


LED 2 ON AT 2100 MS

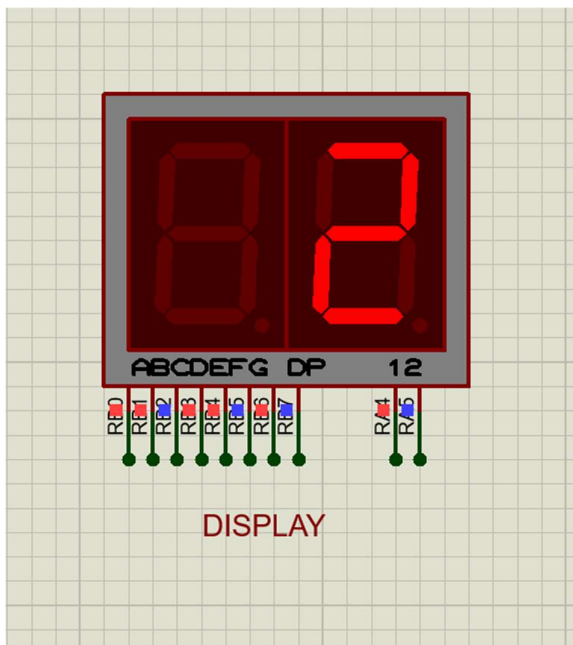


BUTTON 1 ON --- SEGMENT FWD

BUTTON 2 ON – SEGMENT REV

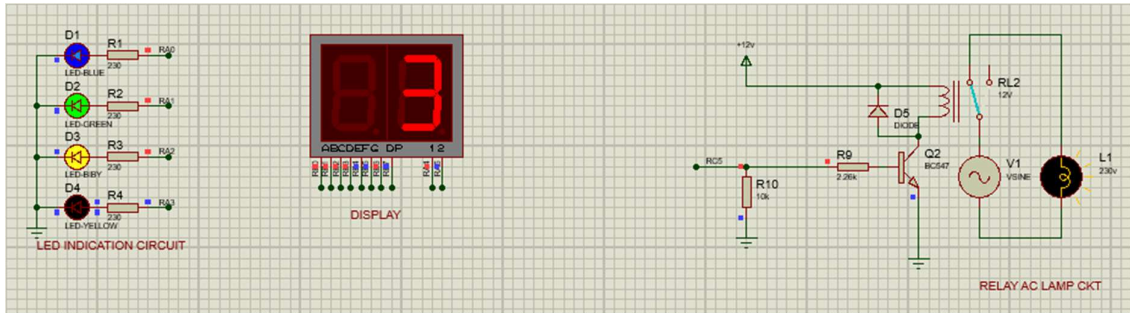

BUTTON 3 ON – LED 3 ON AND AC LAMP ON

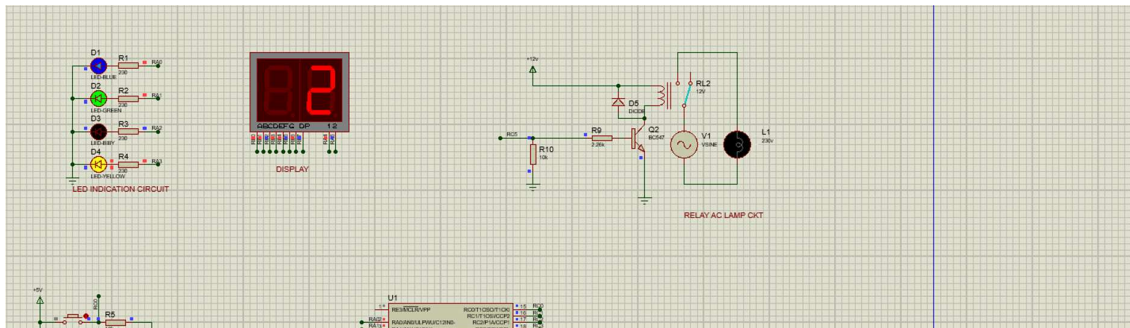

LED 4 ON & AC LAMP OFF